




## MEE 3017 System Modelling and Analysis

## L04 Modelling Electrical Systems

## L04 Modelling Electrical Systems

## Energy Equations in electrical systems

## Energy

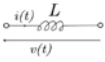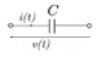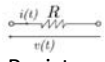
	voltage vs current	voltage vs charge	in terms of charge	
 Inductor	$V_L(t) = L \frac{di(t)}{dt}$	$V_L(t) = L \frac{d^2q(t)}{dt^2}$	$T = E_1 = \frac{1}{2} Li^2$	$T = E_1 = \frac{1}{2} L \dot{q}^2$
 Capacitor	$i(t) = C \frac{dV(t)}{dt}$	$V_C(t) = \frac{q(t)}{C}$	$V = E_2 = \frac{1}{2} CV^2$	$V = E_2 = \frac{1}{2} \frac{1}{C} q^2$
 Resistor	$V(t) = Ri(t)$	$V(t) = R \frac{dq(t)}{dt}$	$\delta w = -Ri\delta q$	$\delta w = -R\dot{q}\delta q$

Virtual Work done by a Voltage Source  $\delta w = -V(t)\delta q$

Dr. Levent ÇETİN

## Elektrik Devrelerinin Modellenmesi:

## Örnek 3.1:

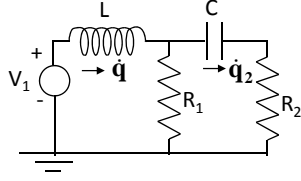
 $R_1$  üzerinden geçen akım =  $\dot{q} - \dot{q}_2$ 
 $V_1$ : Girdi $q$  ve  $q_2$ : Genel yükler

$$E_1 = \frac{1}{2} L \dot{q}^2$$

$$E_2 = \frac{1}{2C} q_2^2$$

$$\delta W = V_1 \delta q - R_1 (\dot{q} - \dot{q}_2) \delta(q - q_2) - R_2 \dot{q}_2 \delta q_2$$

$$= \underbrace{(V_1 - R_1 \dot{q} + R_1 \dot{q}_2)}_{Q_q} \delta q + \underbrace{(R_1 \dot{q} - R_1 \dot{q}_2 - R_2 \dot{q}_2)}_{Q_{q_2}} \delta q_2$$

$$\frac{d}{dt} \left[ \frac{\partial(E_1 - E_2)}{\partial \dot{q}} \right] - \frac{\partial(E_1 - E_2)}{\partial q} = Q_q \Rightarrow L \ddot{q} = V_1 - R_1 \dot{q} + R_1 \dot{q}_2$$

$$\frac{d}{dt} \left[ \frac{\partial(E_1 - E_2)}{\partial \dot{q}_2} \right] - \frac{\partial(E_1 - E_2)}{\partial q_2} = Q_{q_2} \Rightarrow \frac{1}{C} q_2 = R_1 \dot{q} - (R_1 + R_2) \dot{q}_2$$

$$\begin{bmatrix} L & 0 \\ 0 & 0 \end{bmatrix} \begin{Bmatrix} \ddot{q} \\ \ddot{q}_2 \end{Bmatrix} + \begin{bmatrix} R_1 & -R_1 \\ -R_1 & R_1 + R_2 \end{bmatrix} \begin{Bmatrix} \dot{q} \\ \dot{q}_2 \end{Bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & \frac{1}{C} \end{bmatrix} \begin{Bmatrix} q \\ q_2 \end{Bmatrix} = \begin{Bmatrix} V_1 \\ 0 \end{Bmatrix}$$


$$\begin{bmatrix} Ls^2 + R_1s & -R_1s \\ -R_1s & (R_1 + R_2)s + \frac{1}{C} \end{bmatrix} \begin{Bmatrix} q \\ q_2 \end{Bmatrix} = \begin{Bmatrix} V_1 \\ 0 \end{Bmatrix}$$

$$L=3.4 \text{ mH}, C=286 \text{ } \mu\text{F}, R_1=3.2 \text{ } \Omega, R_2=4.5 \text{ } \Omega$$

$$D(s)=0.02618s^3+26.288s^2+11188.81s=0$$

$$\text{Öz değerler: } 0, -502.06 \pm 418.70i (\xi=0.768)$$

## Örnek 3.2

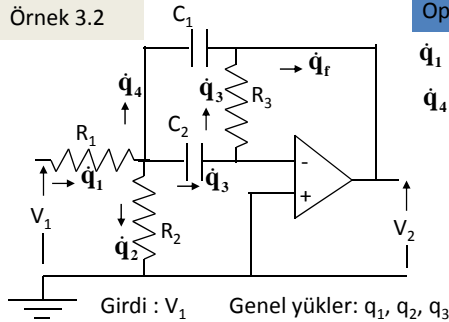Girdi :  $V_1$ Genel yükler:  $q_1, q_2, q_3$ 

Op-amp girişinde direnç çok büyüktür

$$\dot{q}_1 = \dot{q}_2 + \dot{q}_3 + \dot{q}_4 \Rightarrow \dot{q}_4 = \dot{q}_1 - \dot{q}_2 - \dot{q}_3$$

$$\dot{q}_4 + \dot{q}_3 = \dot{q}_f \Rightarrow \dot{q}_f = \dot{q}_1 - \dot{q}_2 - \dot{q}_3 + \dot{q}_3 = \dot{q}_1 - \dot{q}_2$$

$$E_1 = 0$$

$$E_2 = \frac{1}{2C_1} (q_1 - q_2 - q_3)^2 + \frac{1}{2C_2} q_3^2$$

$$\delta W = V_1 \delta q_1 - V_2 \delta(q_1 - q_2) - R_1 \dot{q}_1 \delta q_1$$

$$- R_2 \dot{q}_2 \delta q_2 - R_3 \dot{q}_3 \delta q_3$$

$$\frac{1}{C_1} (q_1 - q_2 - q_3) = V_1 - V_2 - R_1 \dot{q}_1 \quad - \frac{1}{C_1} (q_1 - q_2 - q_3) = V_2 - R_2 \dot{q}_2$$

$$- \frac{1}{C_1} (q_1 - q_2 - q_3) + \frac{1}{C_2} q_3 = -R_3 \dot{q}_3$$

Ayrıca Op-amp ta:  $V_+ = V_- = 0$ 

$$-R_3 \dot{q}_3 = V_2$$

$$\begin{bmatrix} R_1 & 0 & -R_3 \\ 0 & R_2 & R_3 \\ 0 & 0 & R_3 \end{bmatrix} \begin{Bmatrix} \dot{q}_1 \\ \dot{q}_2 \\ \dot{q}_3 \end{Bmatrix} + \begin{bmatrix} \frac{1}{C_1} & -\frac{1}{C_1} & -\frac{1}{C_1} \\ -\frac{1}{C_1} & \frac{1}{C_1} & \frac{1}{C_1} \\ -\frac{1}{C_1} & \frac{1}{C_1} & \frac{1}{C_1} + \frac{1}{C_2} \end{bmatrix} \begin{Bmatrix} q_1 \\ q_2 \\ q_3 \end{Bmatrix} = \begin{Bmatrix} V_1 \\ 0 \\ 0 \end{Bmatrix}$$

$$\begin{bmatrix} R_1 & 0 & -R_3 \\ 0 & R_2 & R_3 \\ 0 & 0 & R_3 \end{bmatrix} \begin{Bmatrix} \dot{q}_1 \\ \dot{q}_2 \\ \dot{q}_3 \end{Bmatrix} + \begin{bmatrix} \frac{1}{C_1} & -\frac{1}{C_1} & -\frac{1}{C_1} \\ -\frac{1}{C_1} & \frac{1}{C_1} & \frac{1}{C_1} \\ -\frac{1}{C_1} & \frac{1}{C_1} & \frac{1}{C_1} + \frac{1}{C_2} \end{bmatrix} \begin{Bmatrix} q_1 \\ q_2 \\ q_3 \end{Bmatrix} = \begin{Bmatrix} V_1 \\ 0 \\ 0 \end{Bmatrix}$$

$$\begin{vmatrix} R_1 s + \frac{1}{C_1} & -\frac{1}{C_1} & -R_3 s - \frac{1}{C_1} \\ -\frac{1}{C_1} & R_2 s + \frac{1}{C_1} & R_3 s + \frac{1}{C_1} \\ -\frac{1}{C_1} & \frac{1}{C_1} & R_3 s + \frac{1}{C_1} + \frac{1}{C_2} \end{vmatrix} = 0$$

$$R_1=15.9 \text{ k}\Omega, R_2=837 \text{ }\Omega, R_3=318 \text{ k}\Omega, C_1=C_2=0.005 \text{ }\mu\text{F}$$

$$\text{Öz değerler: } 0, -628.93 \pm 12561.76i \text{ } (\xi=0.05)$$

